

SECTION - V

9. (a) Build a BCD-to-Seven segment decoder circuit with truth-table. 10
(b) (i) Explain the working of 4-line to 2-line Encoder. 5
(ii) Mention any 5 applications of Decoder. 5
10. (a) Show what would be the output condition for a two input TTL NAND gate for all the input conditions. 10
(b) (i) List the applications of Integrated Circuits. 5
(ii) Define the following parameters of Logic families : 5
(1) Speed (2) Fan in (3) Fan out (4) Power dissipation (5) Noise Margin
-

- (b) (i) Minimize the following Boolean function using K-map : 5

$$Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C + AB\overline{C} + ABC$$
- (ii) Minimize the following Boolean function using K-map : 5

$$F(A, B, C, D) = \sum_1 m(0, 1, 3, 5, 7, 8, 9, 11, 13, 15)$$

SECTION – III

- (a) (i) Explain half-adder with truth-table. 5
 (ii) Explain two bit magnitude comparator with truth-table. 5
- (b) Explain working of a full-subtractor with logic diagram and truth-table. 10
- (a) (i) Give the comparison between serial and parallel adder. 5
 (ii) Mention any 5 applications of comparators. 5
- (b) Explain working of serial binary adder. 10

SECTION – IV

- (a) Explain the working of 4 : 1 multiplexer with logic circuit, symbol and truth-table. 10
- (b) (i) List the applications of demultiplexer. 5
 (ii) Explain the operation of 1 : 2 demultiplexer. 5
- (a) Implement AND and OR Gates using 2 : 1 Multiplexer. 10
- (b) Describe what input conditions would be required to generate the code for the following decimal number in decimal to BCD encoder : 10
- (i) 2
 (ii) 4
 (iii) 8
 (iv) 3
 (v) 7



DIGITAL ELECTRONICS

Time : 3 Hours]

[Max. Marks : 100

- Instructions :** (1) Answer **one** full question from each section.
(2) **One** full question carries 20 marks.

SECTION – I

1. (a) (i) Compare analog and digital signals. 5
(ii) $(10101)_2 - (10111)_2$, calculate using 2's complement method. 5
(b) Perform the following operations : 10
(i) Convert the binary number $(11110101011.0011)_2$ to octal.
(ii) Convert the hexadecimal number $(152A,25)_{16}$ to decimal.
(iii) Convert Gray Code 100111 into Binary number.
2. (a) (i) Give the BCD equivalent for the decimal number 589. 10
(ii) Give the decimal equivalent for the Excess-3 number 010110001001.
(iii) Find the BCD addition between two BCD numbers 0101 and 0110.
(b) (i) State and explain De Morgan's theorem. 5
(ii) Simplify the logical expression using Boolean laws $(A + B)(A + C)$. 5

SECTION – II

3. (a) Define logic gate. Write Symbol, Truth-table and Logic Expression of OR and NAND gates. 10
(b) Realise AND, NOT, OR, NAND gates using only NOR gates. 10
4. (a) (i) Find the SOP minterm expression for canonical form $f = \sum_1 (m_1, m_2, m_3, m_5)$ and write the truth-table. 5
(ii) For the following POS expression, write the truth-table : 5
$$Y = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C}$$

